

## Problem Set #9



1. (12 points) Sketch a block diagram for a magnitude comparator **bit-slice circuit**. Create K-maps to define the bit-slice circuit, and use them to find optimal logic equations. **Sketch the bit-slice circuit.**



2. (12 points) Modify the bit-slice block of problem 1 by removing the logic gates and signals that form the EQ output. Sketch a **"block" circuit diagram** for a **4-bit comparator** that uses the modified bit slice blocks, and add a single gate to form the EQ output from the LT and GT outputs from the MSB (most significant bit).

(4 points) Could you make the bit-slice modules even more efficient by leaving in the EQ logic and removing some other logic? Explain.

3. (10 points) Complete truth tables and K-maps for HA and FA circuits, using XOR patterns where appropriate. Loop minimum SOP equations, and sketch the circuits (assume all inputs and outputs are active high).



Half Adder

| A | B | S | Cout |
|---|---|---|------|
| 0 | 0 |   |      |
| 0 | 1 |   |      |
| 1 | 0 |   |      |
| 1 | 1 |   |      |

  

Full Adder


| A | B | Cin | S | Cout |
|---|---|-----|---|------|
| 0 | 0 | 0   |   |      |
| 0 | 0 | 1   |   |      |
| 0 | 1 | 0   |   |      |
| 0 | 1 | 1   |   |      |
| 1 | 0 | 0   |   |      |
| 1 | 0 | 1   |   |      |
| 1 | 1 | 0   |   |      |
| 1 | 1 | 1   |   |      |

  

4. (10 points) Sketch a block diagram for a full adder using two **half-adder blocks** and an OR gate.

5. (8 points) Sketch an entire **Carry-Propagate-Generate circuit** that can form the **carry-ins** for all four bits of 5-bit CLA.

 6. (20 points) Design a full-subtractor bit-slice circuit (Borrow-Ripple Subtractor). Label the inputs A, B, and Bin, and label the outputs D and Bout. Start by completing the subtraction examples, then complete the truth table and K-maps, and then sketch the circuit.



| A | B | Bin | D | Bout |
|---|---|-----|---|------|
| 0 | 0 | 0   |   |      |
| 0 | 0 | 1   |   |      |
| 0 | 1 | 0   |   |      |
| 0 | 1 | 1   |   |      |
| 1 | 0 | 0   |   |      |
| 1 | 0 | 1   |   |      |
| 1 | 1 | 0   |   |      |
| 1 | 1 | 1   |   |      |

|   |   | B Bin |    |    |    |
|---|---|-------|----|----|----|
|   |   | 00    | 01 | 11 | 10 |
| A | 0 |       |    |    |    |
|   | 1 |       |    |    |    |

D =

|   |   | B Bin |    |    |    |
|---|---|-------|----|----|----|
|   |   | 00    | 01 | 11 | 10 |
| A | 0 |       |    |    |    |
|   | 1 |       |    |    |    |

Bout =

7. (8 points) Complete the number conversions indicated. Note that all binary numbers are two's complement representations.

$$-19_D = \underline{\hspace{2cm}}_B$$

$$10011010_B = \underline{\hspace{2cm}}_D$$

$$10000000 = \underline{\hspace{2cm}}_D$$

$$-101_D = \underline{\hspace{2cm}}_B$$

8. (22 points) Complete the four 2's complement arithmetic problems below assuming that all operations use an adder. Showing both the decimal and binary numbers in each case.

$$\begin{array}{r} 17 \quad 000010001 \\ -11 \quad + \quad 111110101 \\ \hline \end{array}$$

$$\begin{array}{r} -22 \\ +6 \quad + \\ \hline \end{array}$$

$$\begin{array}{r} 35 \\ -42 \quad + \\ \hline \end{array}$$

$$\begin{array}{r} 19 \\ -(-7) \quad + \\ \hline \end{array}$$

$$\begin{array}{r} \quad 10100110 \\ \quad + \quad 11110101 \\ \hline \end{array}$$

Is the answer to the equation on the left correct in 8 bits? Explain.

9. (10 points) Sketch a circuit to convert a 4-bit binary number to its 2's complement representation using only 3 XOR/XNOR gates and 2 AND or OR gates.

10. (8 points) Examine several examples of addition overflow and subtraction underflow, and sketch a circuit below that can output a '1' whenever an addition or subtraction result is incorrect due to underflow or overflow. Assume that both operands and result of the addition and subtraction are N-bits. (Hint: compare the carry in and carry out signals of the most-significant bit).

11. (16 points) Fill in the squares below to show all signal values when "1101" and "1010" are multiplied.

