


Problem Set #5

Revision: 2/3/19

Hand-write Verilog code for the following problems.

 1. (8 points) Complete Verilog code for a multiplexor-based circuit that performs according to the circuit sketch below.

```
module P1 (  
    input A, B, C, D,  
    output Y);  
  
    assign Y =  
  
endmodule
```




2. (8 points) Complete Verilog code to define a circuit that implements the minterm equation:
 $F = \sum m(0, 2, 4, 5, 6)$.

```
module P2 (  
    input  
    output F);  
  
    assign F =  
  
endmodule
```

 3. (8 points) Complete Verilog code to define the circuit shown.

```
module P3 (  
    input A, B, C,  
    output Y);  
  
    assign Y =  
  
endmodule
```



4. (10 points) Complete Verilog code to define a 3:8 decoder. Include all required Verilog statements, including the “module” and “endmodule” statements.
5. (15 points) Complete Verilog code to define a circuit that can shift an 8-bit input data value “D” left or right by up to three bits as defined by the 2-bit “A” input, and drive an output bus “R” with the result (note: if A is ‘00’, then the data simply passes through).

```
module P5 (  
    input [7:0] D, LnR, [1:0] A,  
    output [7:0] R);
```

```
assign Y =
```

```
endmodule
```