

# Problem Set #3

Revision: 2/3/19

1. (58 points) Find minimal equations for the systems shown.

	B	0	1
A			
0		0	1
1		1	1

$F_{SOP} =$   
 $F_{POS} =$

	B	0	1
A			
0		1	1
1		1	0

$F_{SOP} =$   
 $F_{POS} =$

	B	0	1
A			
0		0	1
1		1	0

$F_{SOP} =$   
 $F_{POS} =$

	B	0	1
A			
0		1	0
1		0	1

$F_{SOP} =$   
 $F_{POS} =$

	B	C	00	01	11	10
A						
0			1	0	0	1
1			1	1	0	1

$F_{SOP} =$

	B	C	00	01	11	10
A						
0			1	0	0	1
1			1	1	0	1

$F_{POS} =$

	B	C	00	01	11	10
A						
0			1	0	1	0
1			1	1	1	1

$F_{SOP} =$

	B	C	00	01	11	10
A						
0			1	0	1	0
1			1	1	1	1

$F_{POS} =$

	C	D	00	01	11	10
A	B					
	00		1	0	0	1
	01		1	1	1	1
	11		1	1	0	0
	10		1	0	0	1

$F_{SOP} =$

	C	D	00	01	11	10
A	B					
	00		1	0	0	1
	01		1	1	1	1
	11		1	1	0	0
	10		1	0	0	1

$F_{POS} =$

	C	D	00	01	11	10
A	B					
	00		0	1	1	0
	01		1	0	1	1
	11		1	0	1	1
	10		0	1	1	0

$F_{SOP} =$

	C	D	00	01	11	10
A	B					
	00		0	1	1	0
	01		1	0	1	1
	11		1	0	1	1
	10		0	1	1	0

$F_{POS} =$

$F = \sum m(0, 1, 4, 5)$

$G = \prod M(0, 1, 3, 4, 5, 7, 13, 15)$

	B	C	00	01	11	10
A						
0						
1						

$F_{SOP} =$

	B	C	00	01	11	10
A						
0						
1						

$F_{POS} =$

	C	D	00	01	11	10
A	B					
	00					
	01					
	11					
	10					

$F_{SOP} =$

	C	D	00	01	11	10
A	B					
	00					
	01					
	11					
	10					

$F_{POS} =$

2. (58 points) Loop the logic graphs and find minimal equations for the systems shown below. Circle the equation of the simplest form (SOP or POS), and circle both if they are equal.

	0	1
A		
0	0	1
1	1	φ

$F_{SOP} =$   
 $F_{POS} =$

	0	1
A		
0	1	1
1	1	φ

$F_{SOP} =$   
 $F_{POS} =$

	0	1
A		
0	0	1
1	φ	0

$F_{SOP} =$   
 $F_{POS} =$

	0	1
A		
0	1	0
1	φ	1

$F_{SOP} =$   
 $F_{POS} =$

	B C			
	00	01	11	10
A				
0	1	0	φ	1
1	1	φ	0	1

$F_{SOP} =$

	B C			
	00	01	11	10
A				
0	1	0	φ	1
1	1	φ	0	1

$F_{POS} =$

	B C			
	00	01	11	10
A				
0	1	φ	1	0
1	1	1	1	1

$F_{SOP} =$

	B C			
	00	01	11	10
A				
0	1	φ	1	0
1	1	1	1	1

$F_{POS} =$

	C D			
	00	01	11	10
A B				
00	1	0	φ	1
01	1	φ	1	1
11	φ	1	0	0
10	1	0	0	1

$F_{SOP} =$   
 $F_{POS} =$

	C D			
	00	01	11	10
A B				
00	1	0	φ	1
01	1	φ	1	1
11	φ	1	0	0
10	1	0	0	1

$F_{SOP} =$   
 $F_{POS} =$

	C D			
	00	01	11	10
A B				
00	0	1	1	0
01	1	φ	1	1
11	1	φ	1	1
10	0	1	1	0

$F_{SOP} =$   
 $F_{POS} =$

	C D			
	00	01	11	10
A B				
00	0	1	1	0
01	1	φ	1	1
11	1	φ	1	1
10	0	1	1	0

$F_{SOP} =$   
 $F_{POS} =$

$F = \sum m(0, 1, 4, 5) + \phi(2, 7)$

$G = \prod M(0, 1, 4, 5, 7, 13, 15) + \phi(2, 3, 11, 12, 14)$

	B C			
	00	01	11	10
A				
0				
1				

$F_{SOP} =$   
 $F_{POS} =$

	B C			
	00	01	11	10
A				
0				
1				

$F_{SOP} =$   
 $F_{POS} =$

	C D			
	00	01	11	10
A B				
00				
01				
11				
10				

$F_{SOP} =$   
 $F_{POS} =$

	C D			
	00	01	11	10
A B				
00				
01				
11				
10				

$F_{SOP} =$   
 $F_{POS} =$

3. (20 points) Find minimal SOP and POS equations for the systems shown.

		B C			
	A	00	01	11	10
0		1	1	D	1
1		1	$\bar{D}$	0	1

F<sub>POS</sub>=

		B C			
	A	00	01	11	10
0		D	D+E	E	0
1		$\bar{D}\cdot E$	E	D·E	1

F<sub>SOP</sub>=

		C D			
	A B	00	01	11	10
00		1	$\phi$	$\phi$	1
01		0	E	E	E
11		$\phi$	1	1	0
10		0	$\bar{E}$	$\bar{E}$	0

F<sub>POS</sub>=

		C D			
	A B	00	01	11	10
00		$\bar{E}$	1	$\phi$	F
01		$\bar{E}\cdot F$	$\bar{E}$	1	E·F
11		$\phi$	0	$\phi$	1
10		$\bar{E}$	1	1	F

F<sub>SOP</sub>=

4. (15 points) Find global minimum circuits for the following three logic signal outputs that are all functions of the same three inputs. Show all work.

$$F1 = \sum m (0, 3, 4) \quad F2 = \sum m (1, 6, 7) \quad F3 = \sum m (0, 1, 3, 4)$$