

Problem Set #3

1. (58 points) Find minimal equations for the systems shown.

	B	0	1
A	0	0	1
	1	1	1

$F_{SOP} =$
 $F_{POS} =$

	B	0	1
A	0	1	1
	1	1	0

$F_{SOP} =$
 $F_{POS} =$

	B	0	1
A	0	0	1
	1	1	0

$F_{SOP} =$
 $F_{POS} =$

	B	0	1
A	0	1	0
	1	0	1

$F_{SOP} =$
 $F_{POS} =$

	B C	00	01	11	10
A	0	1	0	0	1
	1	1	1	0	1

$F_{SOP} =$

	B C	00	01	11	10
A	0	1	0	0	1
	1	1	1	0	1

$F_{POS} =$

	B C	00	01	11	10
A	0	1	0	1	0
	1	1	1	1	1

$F_{SOP} =$

	B C	00	01	11	10
A	0	1	0	1	0
	1	1	1	1	1

$F_{POS} =$

	C D	00	01	11	10
A B	00	1	0	0	1
	01	1	1	1	1
	11	1	1	0	0
	10	1	0	0	1

$F_{SOP} =$

	C D	00	01	11	10
A B	00	1	0	0	1
	01	1	1	1	1
	11	1	1	0	0
	10	1	0	0	1

$F_{POS} =$

	C D	00	01	11	10
A B	00	0	1	1	0
	01	1	0	1	1
	11	1	0	1	1
	10	0	1	1	0

$F_{SOP} =$

	C D	00	01	11	10
A B	00	0	1	1	0
	01	1	0	1	1
	11	1	0	1	1
	10	0	1	1	0

$F_{POS} =$

$$F = \sum m(0, 1, 4, 5)$$

$$G = \prod M(0, 1, 3, 4, 5, 7, 13, 15)$$

	B C	00	01	11	10
A	0				
	1				

$F_{SOP} =$

	B C	00	01	11	10
A	0				
	1				

$F_{POS} =$

	C D	00	01	11	10
A B	00				
	01				
	11				
	10				

$F_{SOP} =$

	C D	00	01	11	10
A B	00				
	01				
	11				
	10				

$F_{POS} =$

2. (58 points) Loop the logic graphs and find minimal equations for the systems shown below. Circle the equation of the simplest form (SOP or POS), and circle both if they are equal.

	0	1
A		
0	0	1
1	1	ϕ

$F_{SOP} =$
 $F_{POS} =$

	0	1
A		
0	1	1
1	1	ϕ

$F_{SOP} =$
 $F_{POS} =$

	0	1
A		
0	0	1
1	ϕ	0

$F_{SOP} =$
 $F_{POS} =$

	0	1
A		
0	1	0
1	ϕ	1

$F_{SOP} =$
 $F_{POS} =$

	BC			
	00	01	11	10
A				
0	1	0	ϕ	1
1	1	ϕ	0	1

$F_{SOP} =$

	BC			
	00	01	11	10
A				
0	1	0	ϕ	1
1	1	ϕ	0	1

$F_{POS} =$

	BC			
	00	01	11	10
A				
0	1	ϕ	1	0
1	1	1	1	1

$F_{SOP} =$

	BC			
	00	01	11	10
A				
0	1	ϕ	1	0
1	1	1	1	1

$F_{POS} =$

	CD			
	00	01	11	10
AB				
00	1	0	ϕ	1
01	1	ϕ	1	1
11	ϕ	1	0	0
10	1	0	0	1

$F_{SOP} =$
 $F_{POS} =$

	CD			
	00	01	11	10
AB				
00	1	0	ϕ	1
01	1	ϕ	1	1
11	ϕ	1	0	0
10	1	0	0	1

	CD			
	00	01	11	10
AB				
00	0	1	1	0
01	1	ϕ	1	1
11	1	ϕ	1	1
10	0	1	1	0

$F_{SOP} =$
 $F_{POS} =$

	CD			
	00	01	11	10
AB				
00	0	1	1	0
01	1	ϕ	1	1
11	1	ϕ	1	1
10	0	1	1	0

$F = \sum m(0, 1, 4, 5) + \phi(2, 7)$

$G = \prod M(0, 1, 4, 5, 7, 13, 15) + \phi(2, 3, 11, 12, 14)$

	BC			
	00	01	11	10
A				
0				
1				

$F_{SOP} =$
 $F_{POS} =$

	BC			
	00	01	11	10
A				
0				
1				

	CD			
	00	01	11	10
AB				
00				
01				
11				
10				

$F_{SOP} =$
 $F_{POS} =$

	CD			
	00	01	11	10
AB				
00				
01				
11				
10				

3. (20 points) Find minimal SOP and POS equations for the systems shown.

		B C			
	A	00	01	11	10
0		1	1	D	1
1		1	\bar{D}	0	1

F_{POS}=

		B C			
	A	00	01	11	10
0		D	D+E	E	0
1		$\bar{D} \cdot E$	E	D·E	1

F_{SOP}=

		C D			
	A B	00	01	11	10
00		1	ϕ	ϕ	1
01		0	E	E	E
11		ϕ	1	1	0
10		0	\bar{E}	\bar{E}	0

F_{POS}=

		C D			
	A B	00	01	11	10
00		\bar{E}	1	ϕ	F
01		$\bar{E} \cdot F$	\bar{E}	1	E·F
11		ϕ	0	ϕ	1
10		\bar{E}	1	1	F

F_{SOP}=

4. (15 points) Find global minimum circuits for the following three logic signal outputs that are all functions of the same three inputs. Show all work.

$$F1 = \sum m(0, 3, 4) \quad F2 = \sum m(1, 6, 7) \quad F3 = \sum m(0, 1, 3, 4)$$